

CS-341 Lecture 20

April 20, 2001

Exam on April 24

- Will cover material from Chapter 3
 - Up to section 3.2.4
 - Programmable Logic Devices
 - From Lecture Notes
 - Shifter Design
 - Table 4-2.
 - Carry Lookahead Design from class on April 17. Exercises 14 and 18 relate to this.
(Solutions have been emailed to you.)

Sequential Circuits

- Present state depends on sequence of inputs in the past rather than the current combination of inputs.
 - R-S Latch
 - Clocked R-S Latch
 - D Latch
 - R-S Flip-Flop
 - D Flip-Flop