

CS-341 Lecture 17

April 3, 2001

Combinational Building Blocks

- Decoder
 - n inputs, 2^n outputs
 - Exactly one output true at a time, telling what combination of inputs is true
- Multiplexer
 - n control inputs, 2^n data inputs, one output
 - “Connect” one input to the output
 - Can implement any function of $n+1$ variables
- Half/Full Adder
 - Two data inputs; sum and carry outputs
 - Full adder has carry in

Parallel Adder/Subtractor

- Parallel Adder
 - Link the carry out of one full adder to the carry in of the one to its left.
 - Condition Code values
 - C (carry) is C_{out} of leftmost full adder
 - V (overflow) is *xor* of C_{in} and C_{out} of leftmost full adder
 - N (negative) is Sum output of leftmost full adder
 - Z (zero) is *nor* of all Sum outputs.
- Subtraction
 - *sub* signal negates left operand when asserted
 - Complement all data bits using *xor*
 - Add one by asserting C_0